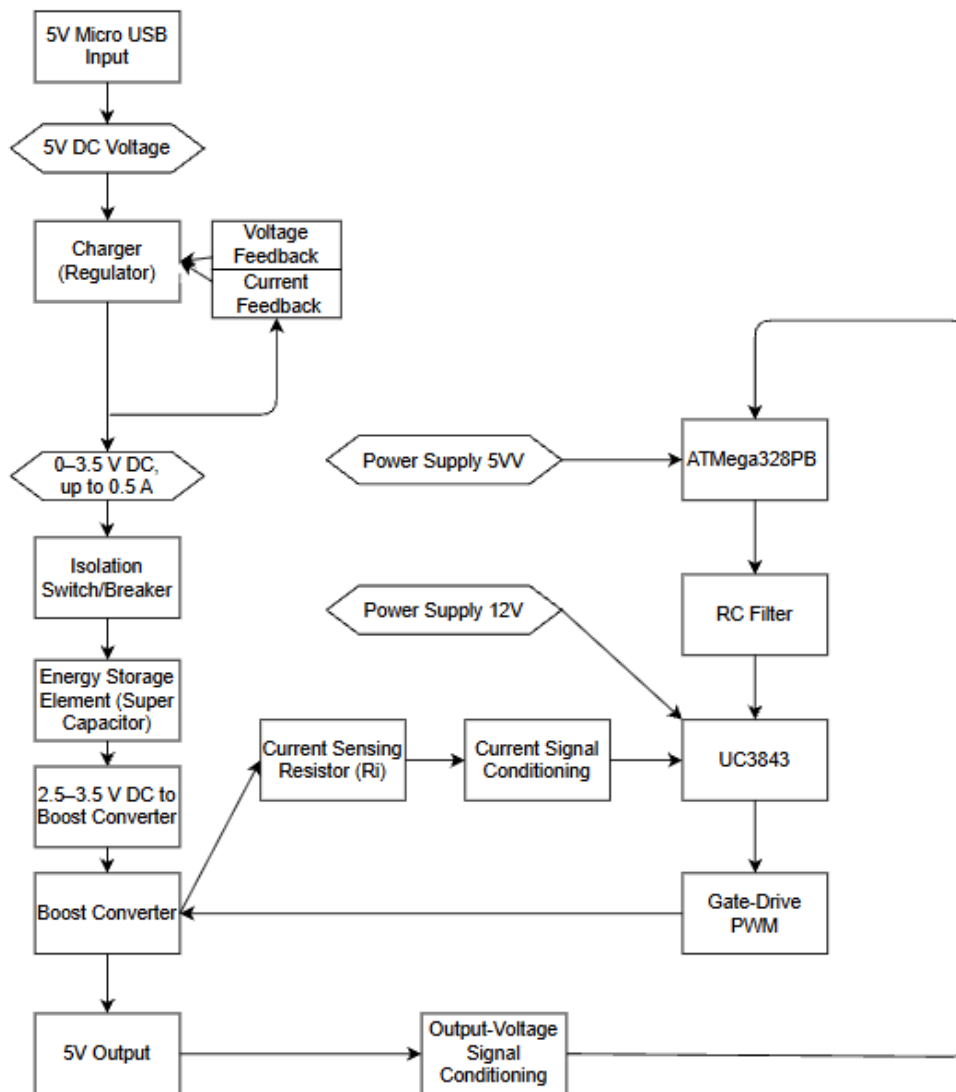




Parts search:


- QBD180 PNP BJT
- Irf9z24n P-Type Mosfet
- LM358 OPAMP
- Super Capacitor 30F or 150F
- UC3843
- ATMega328P

The IRF9Z24N P-channel MOSFET was selected as the switching device because it provides low conduction losses and simple gate driven requirements in a positive supply system. Compared with a BJT, the MOSFET requires negligible steady-state gate current, improving efficiency and reducing the loading on the control circuit. Its low on-resistance minimises voltage drop and power loss during charging and discharging, while its current and voltage ratings provide sufficient margin for the expected operating conditions.

A supercapacitor was selected as the primary energy storage element because it offers extremely high capacitance, rapid charge/discharge capability, and a significantly longer cycle life than rechargeable batteries. The supercapacitor can deliver large transient currents without substantial degradation, making it suitable for a portable power bank application requiring frequent charging and discharging.

The 150 F supercapacitor was selected to maximise stored energy and extend the operating time of the power bank. Although it requires a longer charging period and higher charging current, it better demonstrates the capability of the charging circuit and provides a more practical energy reserve.

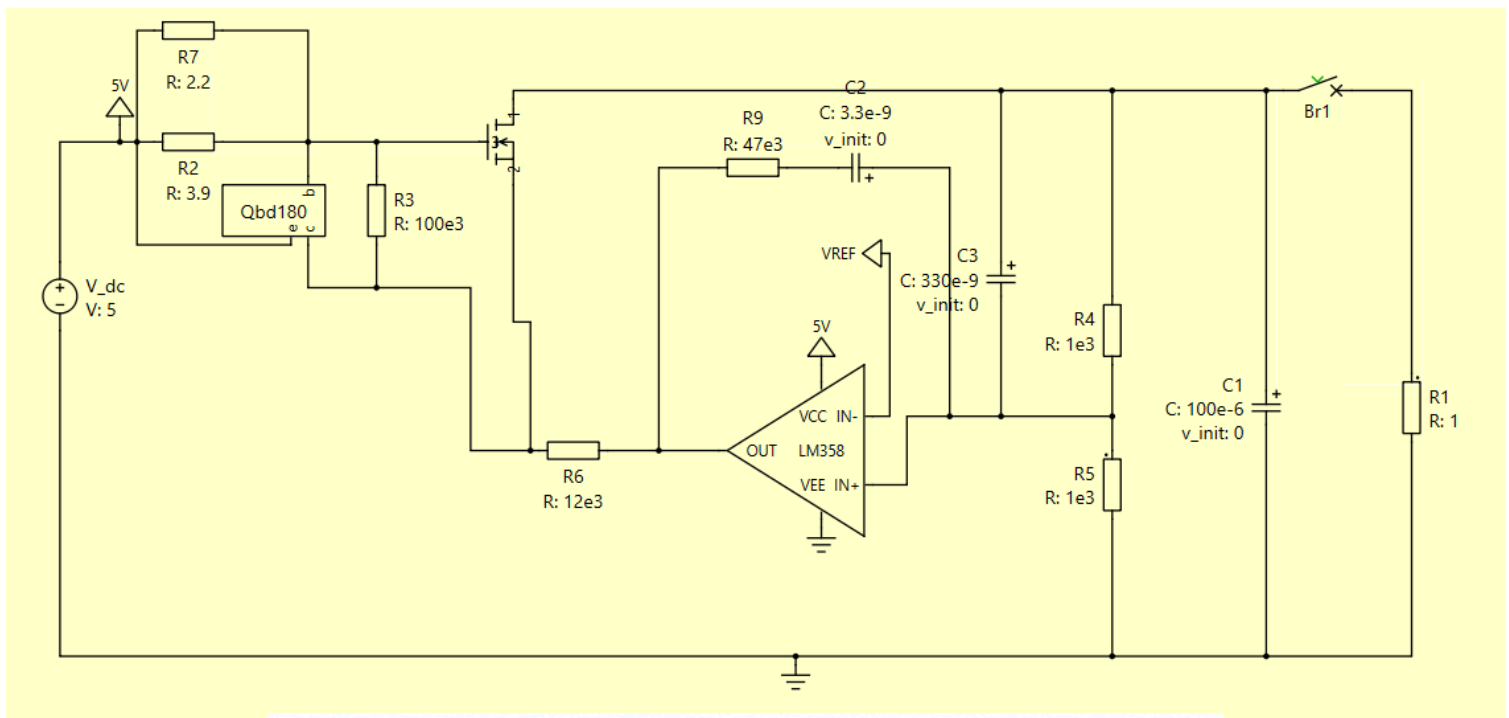P-type equivalent of BD179 BJT which is the BD180 was also used in the current limiting circuit within the charger.



Charger Specifications

Parameter	Value
Input Voltage Range	$2.5 V_{in}$ to $3.5 V_{in}$
Output Voltage	$5 V_{DC}$
Load Regulation	5%
Output Power	0.5 W to 3 W
Output Voltage Ripple	< 50 mV
Switching Frequency	100 kHz
R_{load}	50 ohm

Current limiting:

if input current $> 0.5A$

RJT on when $V_E = V_B + 0.7V(V_{R2})$

$V_{R2} = \text{Input current} \times \text{Resistance}$

$$0.7 = I_{in} \times (2.2k \parallel 13.9k)$$

$$I_{in} = 0.7 / 1.4 = 0.5A$$

R_3 : Pull up resistor

Voltage feedback divider:

$$V_{fb} = 1.75V$$

$$V_{fb} = V_{out} \frac{R_5}{R_4 + R_5}$$

$$V_{fb} = V_{out} \frac{1k}{2k}$$

$$V_{fb} = \frac{V_{out}}{2}$$

$$V_{out} = 3.5V$$

$$\dots\dots$$

Opamp Loop:

LM358 max output = 3.5V

according to the datasheet

Compensation Components:

$$R_9 = 47k, C_2 = 3.3 \times 10^{-9}$$

$$f = \frac{1}{2\pi RC} \rightarrow \frac{1}{2\pi \times 47k \times 3.3 \times 10^{-9}}$$

$$f = 1.03kHz$$

Mosfet:

Mosfet is on when Source > Gate


Source = 5V (4.3 if current limiting)

Gate = 3.5V from opamp max output

Drain = 3.5V from Vref voltage divider

Acts as a variable resistor with 1.5V drop

Preliminary Boost Converter Schematic

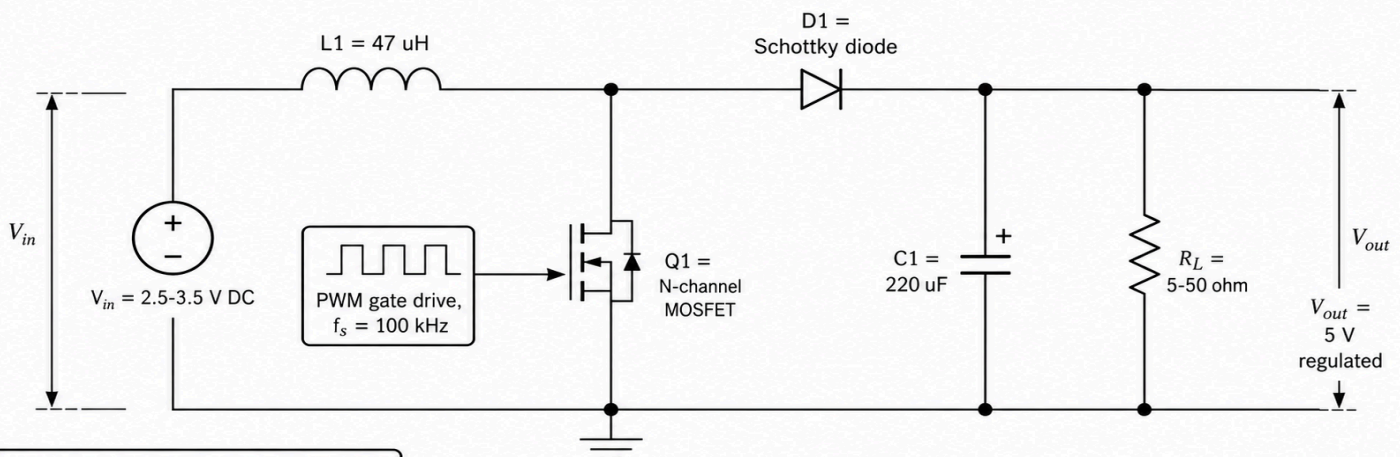

Preliminary Design Values

Output power	: 0.5-5 W
Output current	: 0.1-1.0 A
Duty cycle range	: D = 0.30-0.50
Minimum load	: 5 ohm
Maximum load	: 50 ohm
Target ripple	: < 50 mV

a conventional non-isolated boost converter is proposed to convert the hybrid supercapacitor voltage of 2.5-3.5V to a regulated 5V output. The MOSFET stores energy in L1 during its ON interval and during its OFF interval, L1 transfers energy through D1 to C1 and the load R1

$$V_{out} = \frac{V_{in}}{1-D} \quad D = 1 - \frac{V_{in}}{V_{out}}$$

$$D(2.5V) = 0.5 \quad , \quad D(3.5V) = 0.3$$

$$R_{out} = \frac{V_{out}^2}{P_{out}} = 5-50 \Omega$$

$$L_{min} = \max \left[\frac{a_{out} D(1-D)^2}{2f_s} \right] \approx 37 \mu H$$

$$L = 47 \mu H$$

$$\bullet \text{ At } V_{in} = 2.5V, P_{out} = 5W$$

$$I_{out} = 1A, I_{in} = 2A$$

$$\Delta I_L = \frac{V_{in} D}{L f_s} = 0.866A$$

$$I_{L, peak} = I_{in} + \frac{\Delta I_L}{2} = 2.13A$$

$$C_{o, min} = \frac{I_{out} D}{f_s \Delta V_{out}} = 100 \mu F$$

$$\bullet C_o = 220 \mu F$$

$$\Delta V_{out, ideal} = \frac{I_{out} D}{f_s C_o} = 22.7mV < 50mV$$

Ideal PLECS simulation verifies the topology and initial component values. Closed loop UC3843/ ATmega control and non-ideal device losses will be incorporated during detailed design

Image Generated by

<https://chatgpt.com/>

Thrimawithana, D. J. (2026). *Buck and boost converters* [PowerPoint slides]. Department of Electrical, Computer and Software Engineering, University of Auckland.

DigiKey Electronics. (n.d.). *LIC1325Q3R8157 CDA (Zhifengwei Technology): 150 F, 3.8 V lithium hybrid capacitor*. Retrieved August 4, 2026, from <https://www.digikey.co.nz/en/products/detail/cda-zhifengwei-technology/LIC1325Q3R8157/26118451>

Infineon Technologies. (n.d.). *IRF9Z24N: -55 V single P-channel power MOSFET in a TO-220 package*. Retrieved August 4, 2026, from <https://www.infineon.com/part/IRF9Z24N>

RS Components. (n.d.). *onsemi BD180G transistor, 1 A PNP, 80 V, 3-pin TO-225*. Retrieved August 4, 2026, from <https://nz.rs-online.com/web/p/bipolar-transistors/5450062>

Task Division:

High level system schematic - Bruce/Kyle
Part search & Feasibility study - Alex\Bruce
Literature survey - Bruce/Alex
Calculations/diagrams - Saketh/Kyle